

AG35-Quecopen

Reference Design

Automotive Module Series

Rev. AG35-Quecopen_Reference_Design_V1.4

Date: 2019-05-16

Status: Released



Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:

Quectel Wireless Solutions Co., Ltd.

7th Floor, Hongye Building, No.1801 Hongmei Road, Xuhui District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: info@quectel.com

Or our local office. For more information, please visit:

<http://www.quectel.com/support/sales.htm>

For technical support, or to report documentation errors, please visit:

<http://www.quectel.com/support/technical.htm>

Or email to: support@quectel.com

GENERAL NOTES

QUECTEL OFFERS THE INFORMATION AS A SERVICE TO ITS CUSTOMERS. THE INFORMATION PROVIDED IS BASED UPON CUSTOMERS' REQUIREMENTS. QUECTEL MAKES EVERY EFFORT TO ENSURE THE QUALITY OF THE INFORMATION IT MAKES AVAILABLE. QUECTEL DOES NOT MAKE ANY WARRANTY AS TO THE INFORMATION CONTAINED HEREIN, AND DOES NOT ACCEPT ANY LIABILITY FOR ANY INJURY, LOSS OR DAMAGE OF ANY KIND INCURRED BY USE OF OR RELIANCE UPON THE INFORMATION. ALL INFORMATION SUPPLIED HEREIN IS SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

COPYRIGHT

THE INFORMATION CONTAINED HERE IS PROPRIETARY TECHNICAL INFORMATION OF QUECTEL WIRELESS SOLUTIONS CO., LTD. TRANSMITTING, REPRODUCTION, DISSEMINATION AND EDITING OF THIS DOCUMENT AS WELL AS UTILIZATION OF THE CONTENT ARE FORBIDDEN WITHOUT PERMISSION. OFFENDERS WILL BE HELD LIABLE FOR PAYMENT OF DAMAGES. ALL RIGHTS ARE RESERVED IN THE EVENT OF A PATENT GRANT OR REGISTRATION OF A UTILITY MODEL OR DESIGN.

Copyright © Quectel Wireless Solutions Co., Ltd. 2019. All rights reserved.

About the Document

History

Revision	Date	Author	Description
1.0	2018-06-05	Canice CHEN	Initial
1.1	2018-09-21	Canice CHEN	<ol style="list-style-type: none">Updated schematic designs relating USB.Updated the power supply block diagram in Sheet 3.Updated the notes for “VBAT Design” section in Sheet 4.Updated the schematic designs and the notes in Sheet 8.Added sensor design in Sheet 13.Changed Q0401/Q0402/Q0602/Q1002/Q1501 from digital transistors to MOS transistors and updated their corresponding circuit designs.
1.2	2018-11-21	Canice CHEN	<ol style="list-style-type: none">Added C0101 and C0804 in Sheet 1 and Sheet 8, respectively. And both of them are reserved.Updated the design of SHUT_DOWN and the corresponding notes in Sheet 2.Updated the 3.3V/3.8V power supply designs and the block diagram, and additionally added a note in Sheet 3.Updated the design of VDD_CODEC in Sheet 4.Updated the notes for “MDI Low Pass Filter Schematic” section in Sheet 9.Updated the design of STATUS in Sheet 15.
1.3	2019-01-25	Canice CHEN	<ol style="list-style-type: none">Added a control circuit for the 3.3V DC-DC power supply system in Sheet 3.Updated the note (item 4) and the 3.3V power supply design for eMMC in Sheet 10.Updated R1119 into “NM_0R” (not mounted, 0Ω) in Sheet 11.

			<ul style="list-style-type: none"> 4. Updated sensor IC connection interface into I2C1 interface in Sheet 13. 5. Updated the notes (item 3 and item 4) in Sheet 13.
1.4	2019-05-16	Canice CHEN	<ul style="list-style-type: none"> 1. Enabled HSIC interface (pin 194/195) in Sheet 1. 2. Updated the wakeup pin into pin 61 (GPIO2) in Sheet 1. 3. Updated power supply block diagram for UART in Sheet 3. 4. Added a 1.8V LDO and a control circuit for the UART power supply system in Sheet 4. 5. Updated the UART level translation (IC solution) circuit in Sheet 5. 6. Added pull-down resistors for COEX_UART in Sheet 11. 7. Updated the design for sensor IAM-20680 in Sheet 13. 8. Updated sensor IC connection interface into I2C2 interface in Sheet 13.

Contents

About the Document.....	2
Contents	4
1 Reference Design.....	5
1.1. Introduction	5
1.2. Schematics	5

1 Reference Design



1.1. Introduction

This document provides reference designs of Quectel AG35-Quecopen module, including the design of power supply, UART, (U)SIM, USB, sensor, eMMC, Ethernet transceiver and more interfaces.

1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.


Module Interfaces

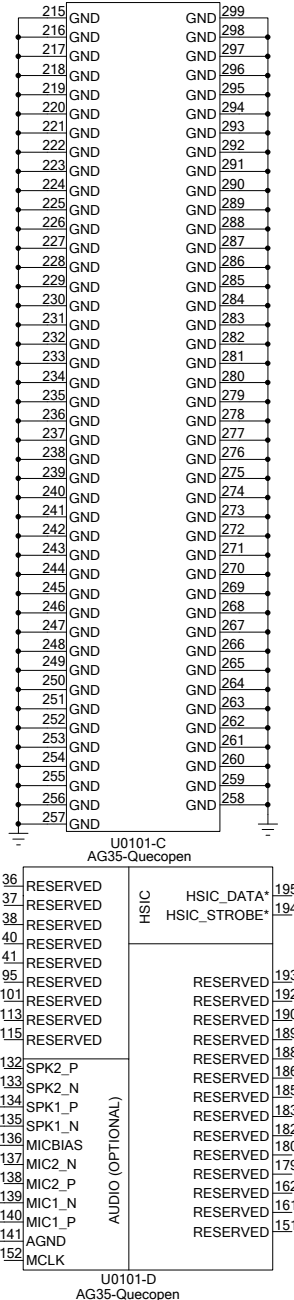 

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 1 OF 15		DATE 2019/5/16

MCU Interfaces

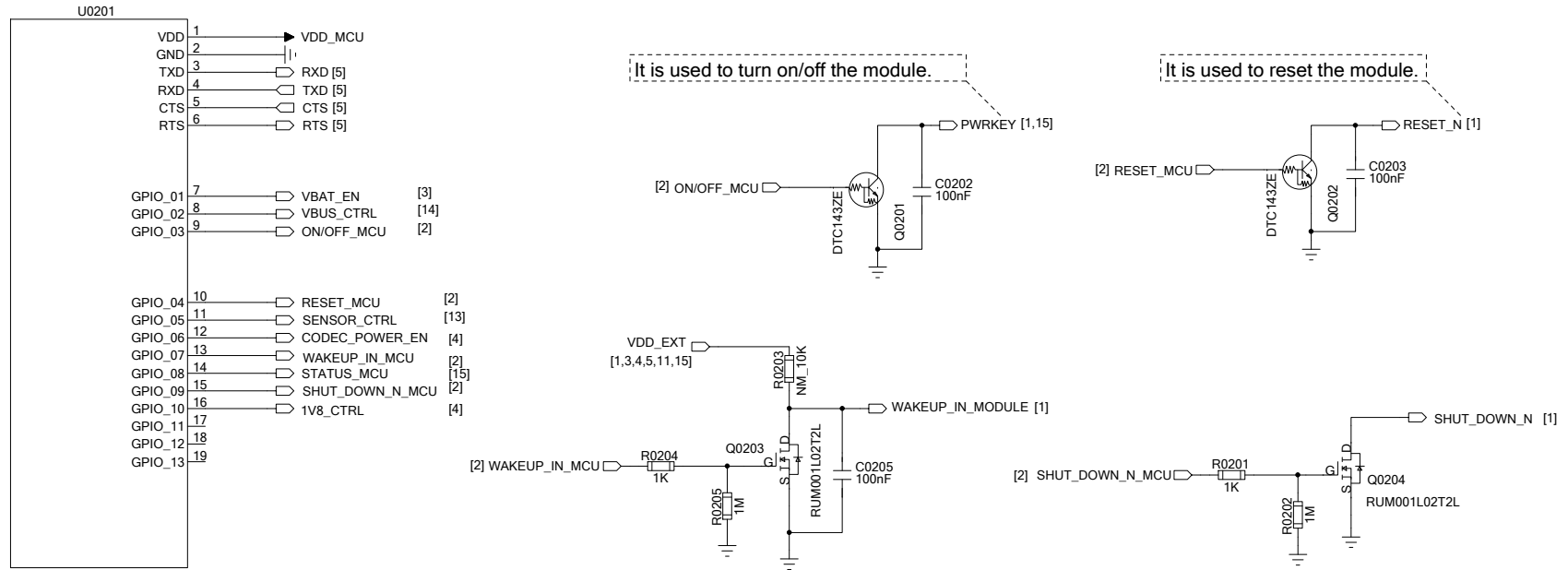


Notes:

1. U0201 represents customer's MCU.
2. Transistor circuits (Q0201~Q0204) are used for level translation.
3. SHUT_DOWN_N_MCU is an emergency option to shut down the module.
When it is at high level, the module will be shut down.

Quectel Wireless Solutions


DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 2 OF 15		DATE 2019/5/16

 A DC-DC converter is used to convert a high input voltage into 5V, 3.8V and 3.3V outputs, and then the LDOs will generate 1.8V typical voltages.




Power Supply Design (Part 2)

VBAT Design

 


- Notes:
- 1. The zener diode D0401 will generate about 3uA leakage current under 3.8V power supply. Therefore, if VBAT is stable, then D0401 can be reserved and not mounted.
 - 2. The power supply must be able to provide sufficient current up to 2A or more.
 - 3. VBAT should be routed in star mode to VBAT_BB and VBAT_RF pins.
 - 4. The recommended operating voltage of VBAT is 3.3V~ 4.3V.

AF20 Power Supply

 


- Note:
- The RC circuit, which is assembled with R0417 and C0419, is used to delay the start-up of MOSFET switch circuit.

UART Level Translation Power Supply

 

PCM Codec Power Supply

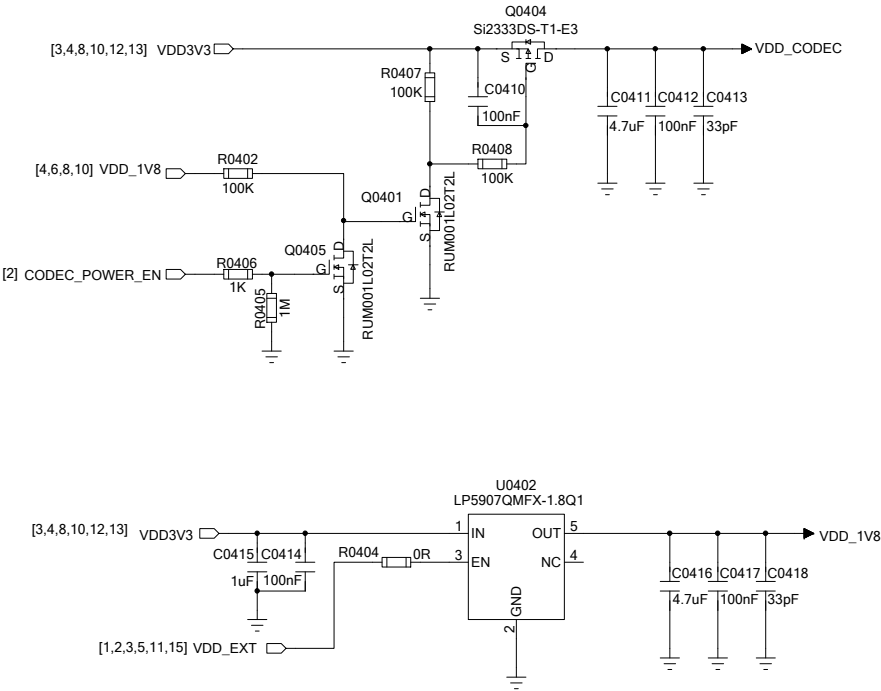

- Note:
- CODEC_POWER_EN must be at low level to ensure normal work of PCM codec.
If VDD_CODEC power supply needs to be switched off, please keep CODEC_POWER_EN at high level.

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 4 OF 15		DATE 2019/5/16

D

1




A



Analog Design (PCM Interface)


Audio - Codec Design

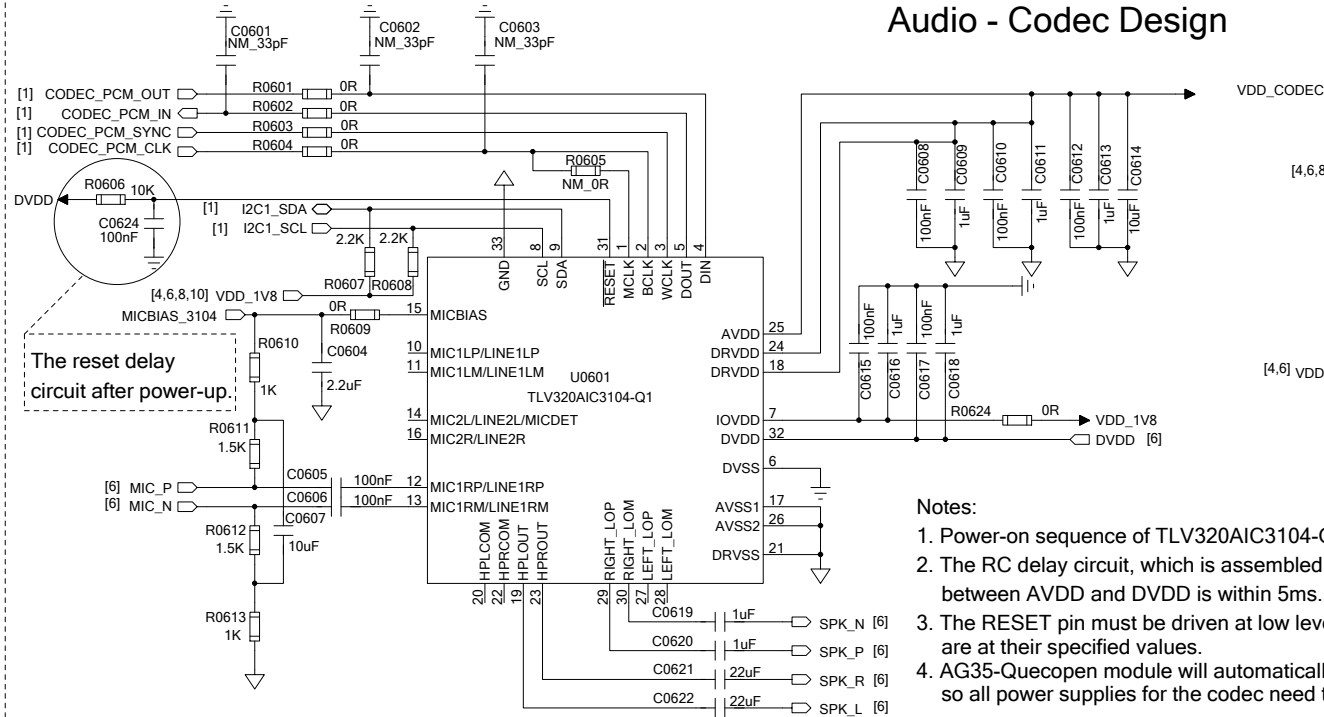

Notes:

1. Power-on sequence of TLV320AIC3104-Q1: IOVDD → AVDD/DRVDD → DVDD → Software Initialization
2. The RC delay circuit, which is assembled with C0623 and R0616, is used to ensure that the power-on time difference between AVDD and DVDD is within 5ms. For more details, please refer to TLV320AIC3104-Q1 datasheet.
3. The RESET pin must be driven at low level for at least 10ns after all power supplies for TLV320AIC3104-Q1 are at their specified values.
4. AG35-Quecopen module will automatically initialize the codec via I2C1 interface after it is turned on successfully, so all power supplies for the codec need to be turned on before that.


Audio - Earphone Application

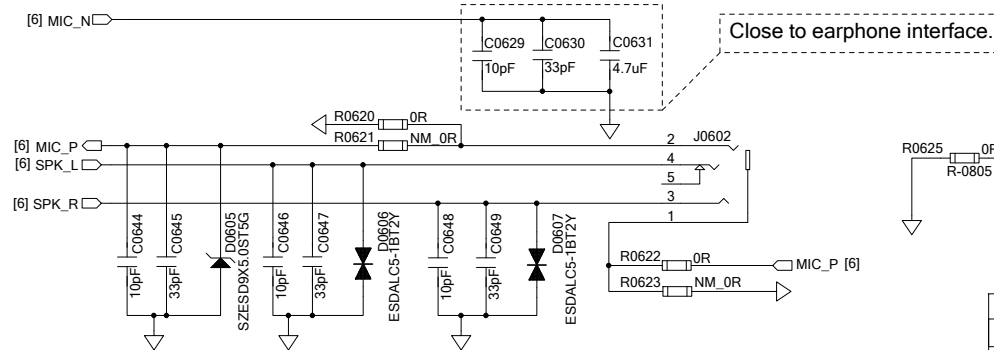

Notes:

1. The analog output only drives earphone and handset. For larger power loads such as speakers, the design for an audio power amplifier should be added.
2. The maximum capacitive loading for speaker is 330pF and the maximum capacitive loading for microphone is 250pF.
3. The analog GND should be connected to the main GND via the 0Ω resistor R0625.

Audio - Handset Application

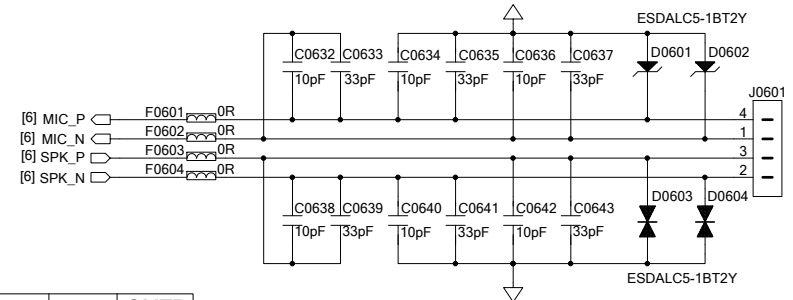


	CTIA	OMTP
R0621/R0623	NM	M
R0620/R0622	M	NM

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 6 OF 15		DATE 2019/5/16

Analog Interface (Optional)


Audio - Handset Application

 

- Notes:
- 1. The analog output only drives handset. For larger power loads such as speakers, the design for an audio power amplifier should be added.
 - 2. The maximum capacitive loading for speaker is 330pF and the maximum capacitive loading for microphone is 250pF.
 - 3. The analog output and input interface circuits should close to AG35-Quecopen.
 - 4. The analog GND should be connected to the main GND via the 0Ω resistor R0701.

Quectel Wireless Solutions		
DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 7 OF 15		DATE 2019/5/16

Ethernet Transceiver Design (Part 1)

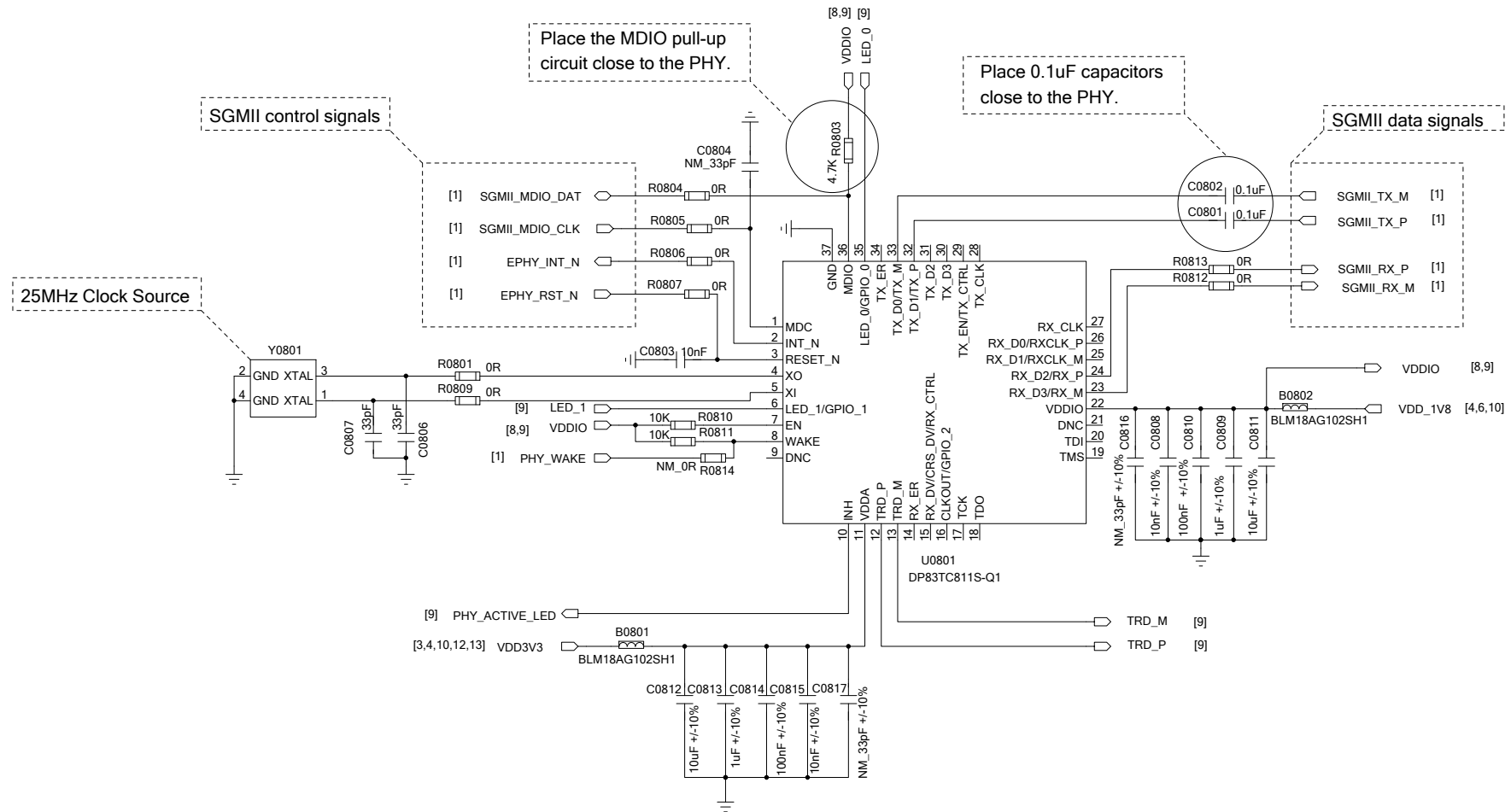


- Notes:
1. The PHY address is 0x00 by default.
 2. This reference design is configured for Physical Medium Attachment Slave Mode.
 3. Place the clock source near the XI and XO pins, and it is recommended to keep 50Ω impedance control for the control signals.
 4. TRD_M and TRD_P, TX_M and TX_P, RX_M and RX_P must be routed with 100Ω±10% differential impedance control, and keep the reference ground complete and integral.
 5. Keep the maximum trace length of data signals less than 25mm and keep the intra-pair length matching less than 0.5mm. In order to avoid crosstalk, it is recommended to maintain the intra-lane spacing of control signals and intra-pair spacing of data signals both as three times of the trace width.
 6. It is important to route the data and control signals with total grounding, and keep them away from sensitive signals. The differential pairs are recommended to be routed on inner-layer of PCB.
 7. The Ethernet transceiver is recommended to be designed on the same PCB on which the module is mounted, and at least a 4-layer PCB should be used.

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 8 OF 15		DATE 2019/5/16

Ethernet Transceiver Design (Part 2)

MDI Low Pass Filter Schematic

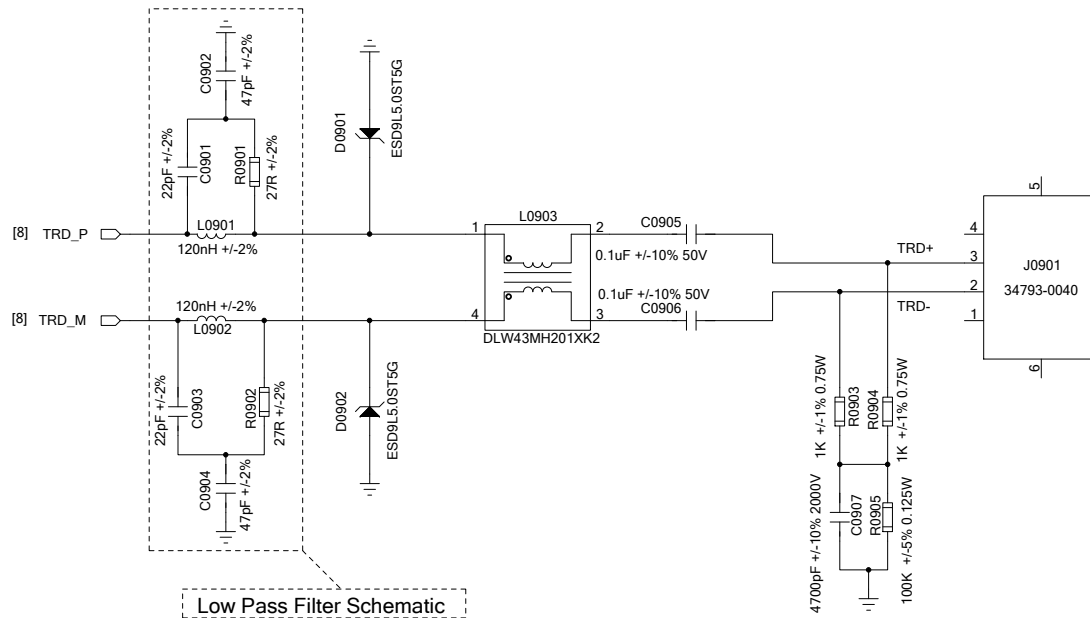


Low Pass Filter Schematic

Notes:


1. Create a top-layer copper pour keepout under the common-mode choke.
2. The low pass filter schematic is already available inside the PHY chip, and the external circuits and ESD are optional.
3. The impedance of MDI TRD_M and TRD_P traces should be controlled as 100Ω while routing.

Indicators

Link Rate Indication LEDs

 

Operation Status Indication LED

 



Note:

The operation status indication LED will be turned on when the ethernet transceiver enters into sleep or disabled mode.

Quectel Wireless Solutions



DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 9 OF 15	DATE 2019/5/16	

eMMC Design

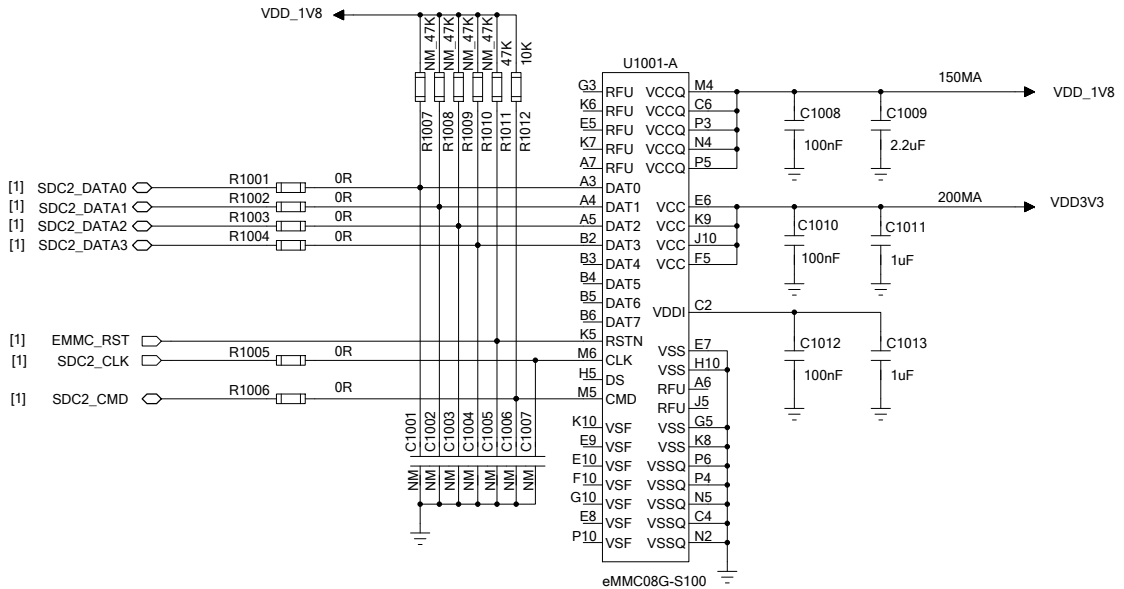 

AF20 Design

AF20 Antenna Circuit

 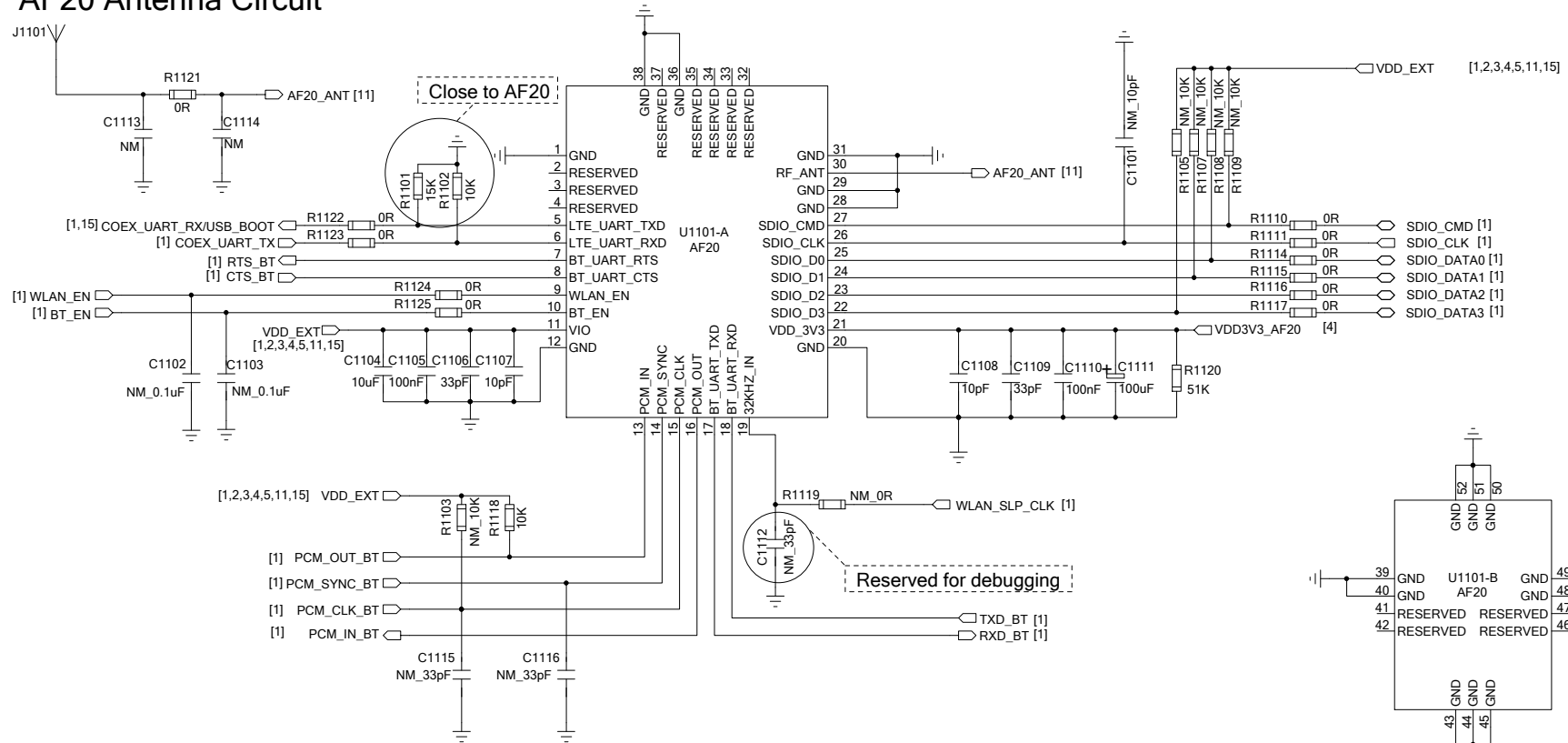

Notes:


1. Keep all RESERVED and unused pins unconnected.
2. The impedance of the SDIO data signal traces must be controlled as 50Ω when routing.
3. SDIO data lines should be shielded by ground; SDIO_CMD and SDIO_CLK signal lines should be shielded by ground separately.
4. It is recommended to use PI type AF20 antenna circuit, thus ensuring convenient subsequent debugging.
5. The impedance of RF signal trace must be controlled as 50Ω when routing.

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 11 OF 15		DATE 2019/5/16


Antenna Interface and Antenna Detection Circuit Designs

 Main Antenna Interface and Detection Circuit (Normal)



Note:
In order to achieve successful antenna status detection, the main antenna is recommended to integrate an 8~13KΩ resistor (R_{in}) to GND. And the typical value for the resistor is 10KΩ.

 Rx-diversity Antenna Interface and Detection Circuit (Normal)




Notes:
1. In order to achieve successful antenna status detection, the Rx-diversity antenna is recommended to integrate an 8~13KΩ resistor (R_{in}) to GND. And the typical value for the resistor is 10KΩ.
2. The Rx-diversity reception function is ON by default. If Rx-diversity antenna is not used, there is a need to use AT command to turn off Rx-diversity reception.

Main / Rx-diversity Antenna Status Indication					
Antenna Status	Open	R _{in} =8KΩ	R _{in} =10KΩ	R _{in} =13KΩ	Short to GND
ADC Value	1.7V	0.7V	0.8V	0.9V	0V
Status Indication	Open	Normal	Normal	Normal	Short to GND

Notes:
1. It is recommended to use PI type Main/Rx-diversity antenna circuit, thus ensuring convenient subsequent debugging.
2. The impedance of the RF signal traces must be controlled as 50Ω when routing.
3. ADC value can be read by AT+QADC=<port>. For more details, please refer to *Quectel_AG35_AT_Commands_Manual*.
4. Three kinds of antenna status are designed to be detected: Normal, Short to GND and Open.
5. The antenna connection status is judged by the ADC feedback value.

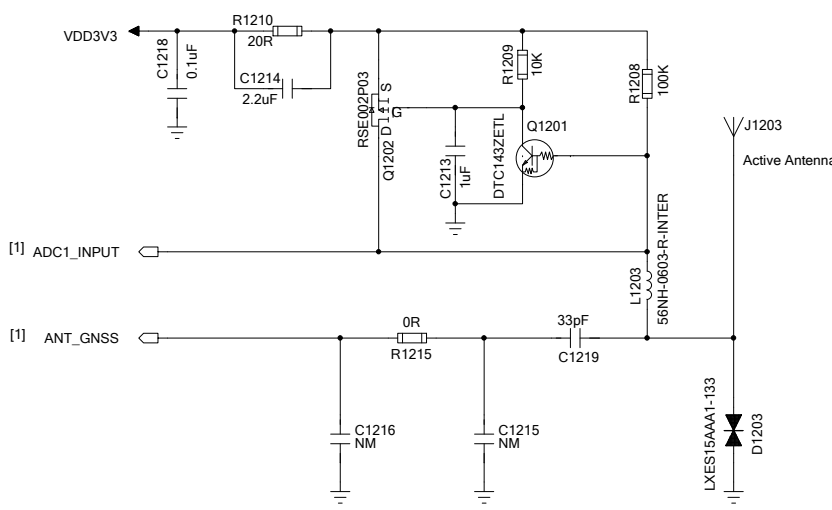GNSS Antenna Interface and Detection Circuit (Normal)




GNSS Antenna Status Indication			
Antenna Status	Open	Normal	Short to GND
ADC Value	VDD_3V3	VDD_3V3-R1210*I_GNSS	0V

Notes:
1. A low power active antenna is recommended to be selected.
2. An external LDO can be selected to supply power for active antenna.
3. VDD_3V3 is the power supply for active antenna, and I_GNSS is the working current of active antenna.
4. The active antenna power supply shall not exceed VBAT voltage of the module. And ADC0 or ADC1 shall be selected for ADC value detection.


Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 12 OF 15		DATE 2019/5/16

Sensor Design (Optional)

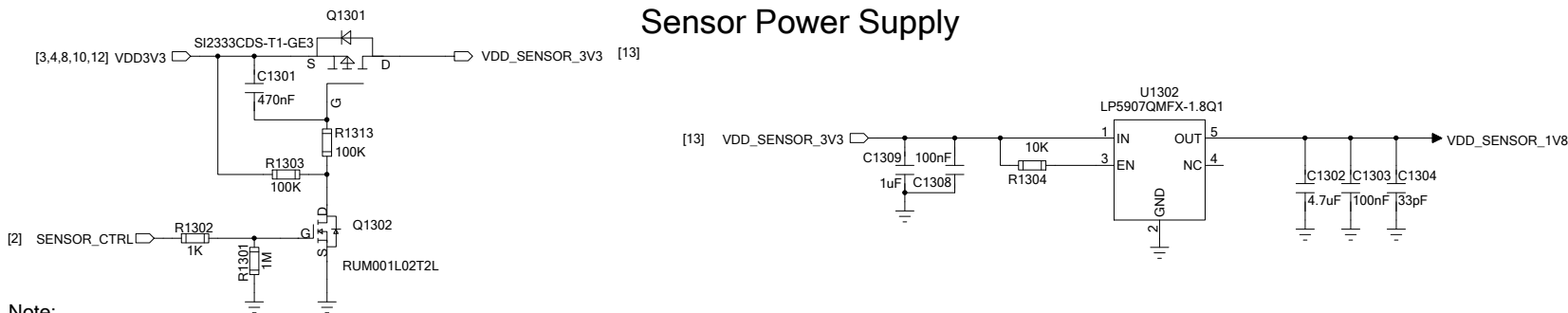

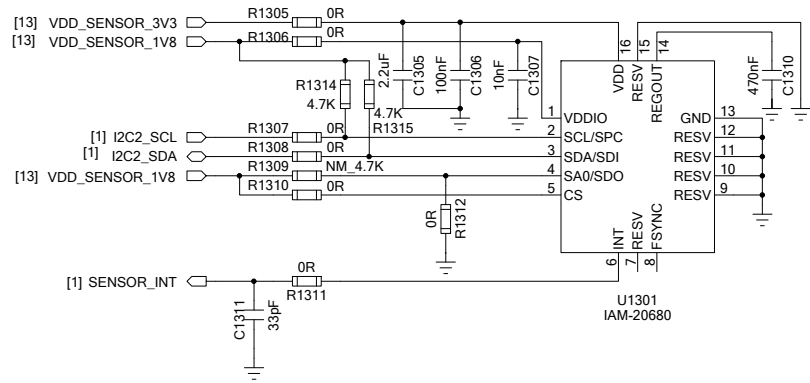Note:
When SENSOR_CTRL is at high level, VDD_SENSOR_3V3 will be powered on.





IAM-20680 I2C Addresses		
Connection	GND (Default)	1V8
SA0	0x68(1101000)	0x69(1101001)

- Notes:
1. The device will come up in sleep mode upon power-up.
 2. If DR function is used, it is recommended to multiplex the UART1 interface into SPI2 interface for communication with MCU.
 3. The module also supports sensor models such as SMI-130 from Bosch and ASM330LHH from STMicroelectronics.

Quectel Wireless Solutions		
DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 13 OF 15		DATE 2019/5/16

USB Interface

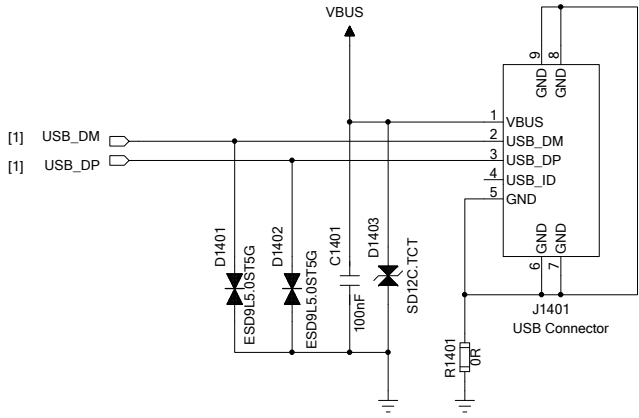
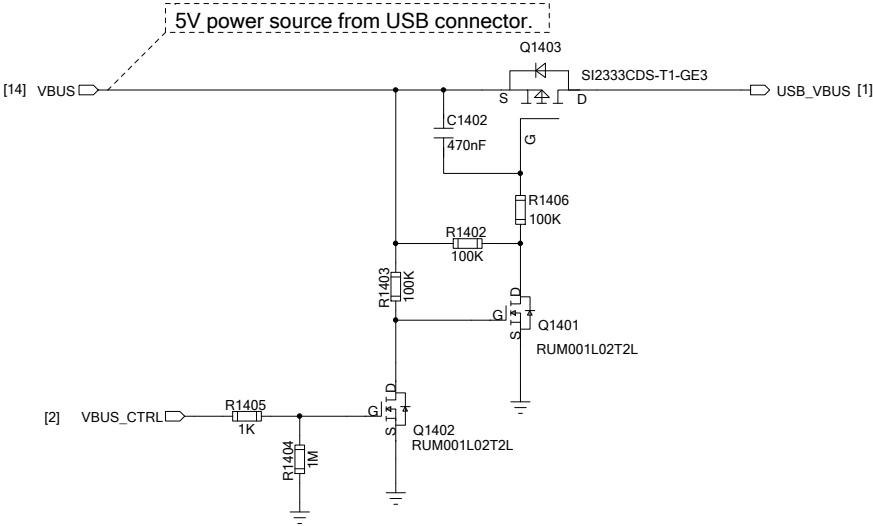


- Notes:
- 1. AG35-Quecopen can work as a USB device or USB host and supports Full Speed and High Speed modes.
The USB_VBUS pin of AG35-Quecopen should be powered by a 5V power system for USB detection.
 - 2. USB interface can be used to debug and upgrade firmware.
 - 3. Please note that the junction capacitance of ESD protection devices on USB data lines might influence the signal. Typically, the capacitance should be less than 2pF.
 - 4. USB_VBUS should be controllabe by USB host.
VBUS_CTRL is used to turn on/off USB_VBUS power supply by MCU, and at low level by default.
When VBUS_CTRL is at high level, USB_VBUS will be switched off.

Quectel Wireless Solutions		
DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 14 OF 15		DATE 2019/5/16

Indicators and Test Points


Indicators

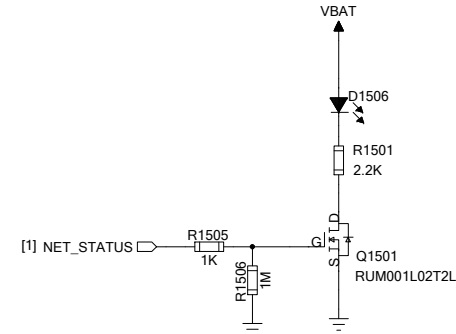 

Notes:

1. The STATUS is an open drain output pin, and its drive current is less than 0.15mA.
2. For more details about STATUS and NET_STATUS, please refer to *Quectel_AG35-Quecopen_Hardware_Design*.
3. If minimized power consumption is required when the device is in sleep mode, it is recommended to replace the power supply of indicators with a controllable one, and switch off the power when the module enters sleep mode.


Reserved Test Points

 

Notes:

1. Debug UART interfaces are reserved for software debugging.
2. The debug interface supports 1.8V power domain.
A level translator should be used if the power domain of customers' application is 3.3V.

USB_BOOT for Download

 

Note:

COEX_UART_RX/USB_BOOT is kept open by default. When it is at high level during module power-up, the module will be forced into download mode directly.

Quectel Wireless Solutions

DRAWN BY Canice CHEN	PROJECT AG35-Quecopen	TITLE Reference Design
CHECKED BY Yeoman CHEN	SIZE A2	VER 1.4
SHEET 15 OF 15		DATE 2019/5/16